



## CSC 220: Computer Organization

### Lab Project

**Due Date: Sunday 7 April**

**Project Description:** The aim of this project is to design the 4-bit Function Unit Combining Arithmetic Logic Unit (ALU) and a Shifter that can perform the operations given in table 1 below.

- Use X and Y as 4 bits input and F as 4 bits output as shown in Figure 1.
- S0,S1,S2 and S3 represent the selction code in the operation set table
- Three statue bits V (over flow), C (carry), N (negative) and are related to arrithmetic operations and statue bit Z (zero) is relataed to both arrithmetic and logic operation.
- Test your designed Function Unit with necessary tables.

**Marking:** Total marks for the project is five (5). Each student needs to submit the project and demonestrate it individually.

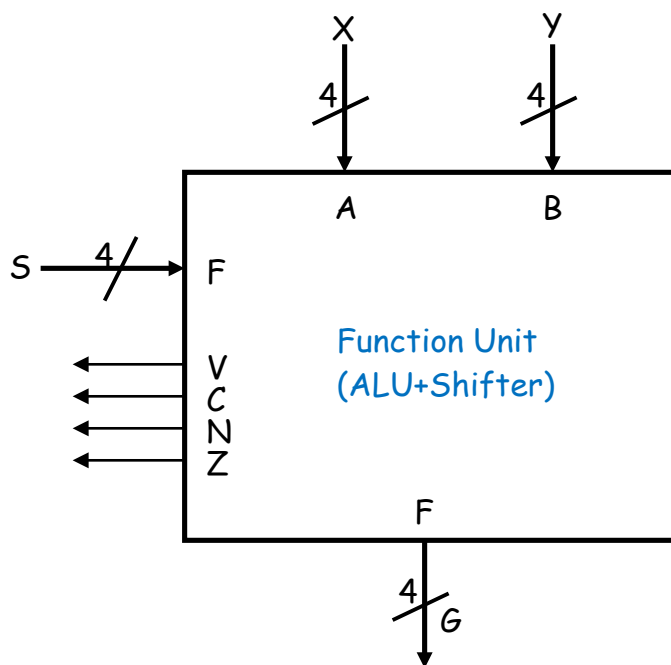


Figure 1: Block diagram of 4-bit Function Unit

**Table1 : Set of operations**

S3	S2	S1	S0	Operation
0	0	0	0	$G=X$
0	0	0	1	$G=X+1$
0	0	1	0	$G=2*X$
0	0	1	1	$G=2*X+1$
0	1	0	0	$G=X+Y'$
0	1	0	1	$G=X+Y'+1$
0	1	1	0	$G=X-1$
0	1	1	1	$G=X$
1	0	0	0	$G=X \text{ AND } Y$
1	0	0	1	$G=X \text{ XOR } Y$
1	0	1	0	$G=X \text{ OR } Y$
1	0	1	1	$G=X'$
1	1	0	0	$G=Y'$
1	1	0	1	$G= \text{Logical Shift left } X$
1	1	1	0	$G=Y$
1	1	1	1	$G=\text{Rotate Shift Right } Y$

**Submission:** (Upload your project on LMS before Sunday 7 April -11:59 p.m)

You need to submit the following:

1. Your circuit in logisim file.
2. A pdf file contains: A screen shot of your circuit and test cases for each operation. In each case you need to specify the value of S, X and Y with the corresponding output as following:

Input				Operation	Input		Expected output				
S <sub>3</sub>	S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>		X	Y	G	C	V	N	Z
0	1	0	0	$G=X+Y'$	0001	0010	1110	0	1	1	0
0	1	0	0		1010	1001	0000	1	1	0	1

**Submission instructions:**

1. Put your files (circuit + PDF) in one folder.
2. Name the folder as: your name\_LABInstructor.
3. Compress the folder and upload it.